

Lab #4: Basic Computer Organization

CEG 2136 – Computer Architecture

Fall 2022

School of Electrical Engineering and Computer Science

University of Ottawa

Course Coordinator: Voicu Groza

Teaching Assistants: Varun

Hamideh

Shruthi

Group #19

Liam Julien 300251443

Santiago Martinez-Barrera 300234735

Experiment Date: November 9, 2022

Submission Date: December 7, 2022

Objective:

- The point of this lab is to analyze the structure of a basic computer, we will devise design, implement, simulate and test the control unit on Altera platform. The design should function in simulation and on the board if everything is well done.

Equipment and Components

- Quartus II
- Altera DE2-115 board with USB-Blaster cable and Power supply 12 VDC, 2A

Theory

The first part of the lab was analyzing the design of the basic computer that was given to us. To properly understand the lab, we had to complete the prelab questions. The prelab questions tested our knowledge of the basic background information of the basic computer. The second part tested our ability to formulate equations using tables of values.

Design

- **Presentation of Design:**

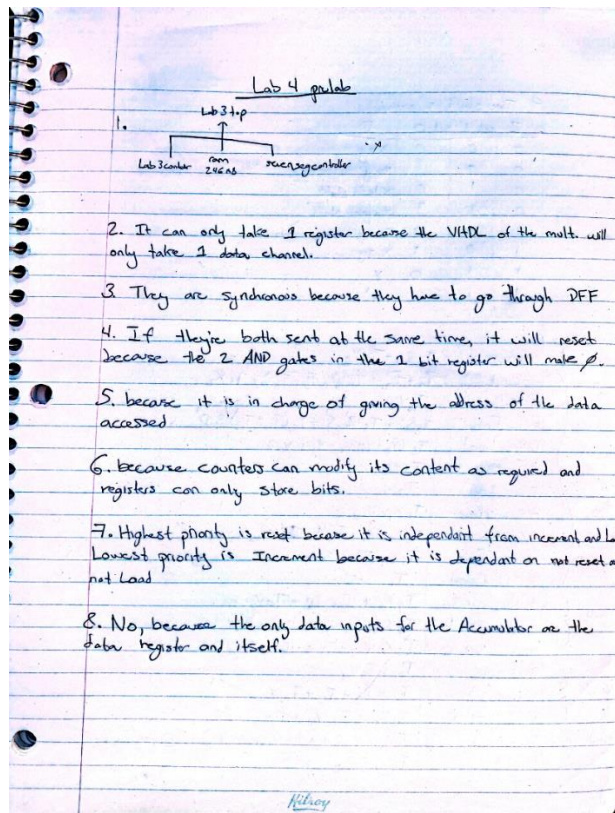


Figure 1: Pre-Lab for the Hardware Section

9. The shift is arithmetic

sel 2	sel 1	sel 0	D
0	0	0	$x+y$
0	0	1	$x+y'$
0	1	0	x left shift
0	1	1	x right shift
1	0	0	$x \cdot y$
1	0	1	$x \div y$
1	1	0	y
1	1	1	x'

mem	memwrite	$T_9 Y_4 + T_{10} Y_6$
CPU Reg	AR-Load	$T_0 + T_2 + IR_6' (T_8 + T_6) + T_1 X_2$
	PC-Load	$T_8 Y_5$
	PC-Inc	$T_2 S' + T_5 IR_6' S' + Y_6 (T_{11} + T_{12}) S' D_{11-7}'$
	DR-Load	$T_8 (Y_0 + Y_1 + Y_2 + Y_3 + Y_4)$
	DR-Inc	$T_9 Y_6$
	IR-Load	T_3
	AC-Clear	$T_5 X_1 IR_0$
	AC-Load	$T_5 X_1 IR_1 + T_5 X_1 IR_2 + T_5 X_1 IR_3 + T_9 (Y_0 + Y_1 + Y_2 + Y_3)$
	AC-Inc	$T_5 X_1 IR_4$
	OUTD-Load	T_1
ALU	ALU_sel 2	$T_9 Y_0 + T_5 X_1 IR_1 + T_9 Y_3$
	ALU_sel 1	$T_5 X_1 (IR_1 + IR_2 + IR_3) + T_9 Y_3$
	ALU_sel 0	$T_5 X_1 IR_3 + T_5 X_1 IR_4 + T_9 Y_2$
BUS	BUS sel 2	$T_0 + T_9 Y_4$
	BUS sel 1	$T_0 + T_2 + T_5 + T_{10} Y_6$
	BUS sel 0	$T_8 Y_5 + T_{10} Y_6 + T_5 Y_4$
control unit	SC-Clear	$T_5 X_1 + T_5 (Y_0 + Y_1 + Y_2 + Y_3 + Y_4) + T_2 Y_5 + T_{12} Y_6$
	Halt	$T_5 X_1 IR_5$

Figure 2: Pre-Lab for the Hardware Section (Equations)

CEG2136 - Software PreLab

7.1

2)

$AC \leftarrow \text{Counter}$

$AC \leftarrow AC'$

$\text{Counter} \leftarrow \text{Counter} + 1$

If $\text{Counter} = 0$; then $PC \leftarrow PC + 1$ and HLT else

$PC \leftarrow 20$

$AC \leftarrow M[X]$

$AC \leftarrow AC + M[Y]$

$M[Z] \leftarrow AC$

$AC \leftarrow X$

$AC \leftarrow AC + 1$

$X \leftarrow AC$

$AC \leftarrow AC + 1$

$Y \leftarrow AC$

$AC \leftarrow AC + 1$

$Z \leftarrow AC$

Loop back to line 4

3) It sums the operands pointed by X and Y and stores their sums in the address pointed to by Z. It also calculates a fibonacci sequence of size 12.

4) Its practical because as the pointers increment, you can still access the new memory slots.

Althay

Figure 3: Pre-Lab for the Software Section

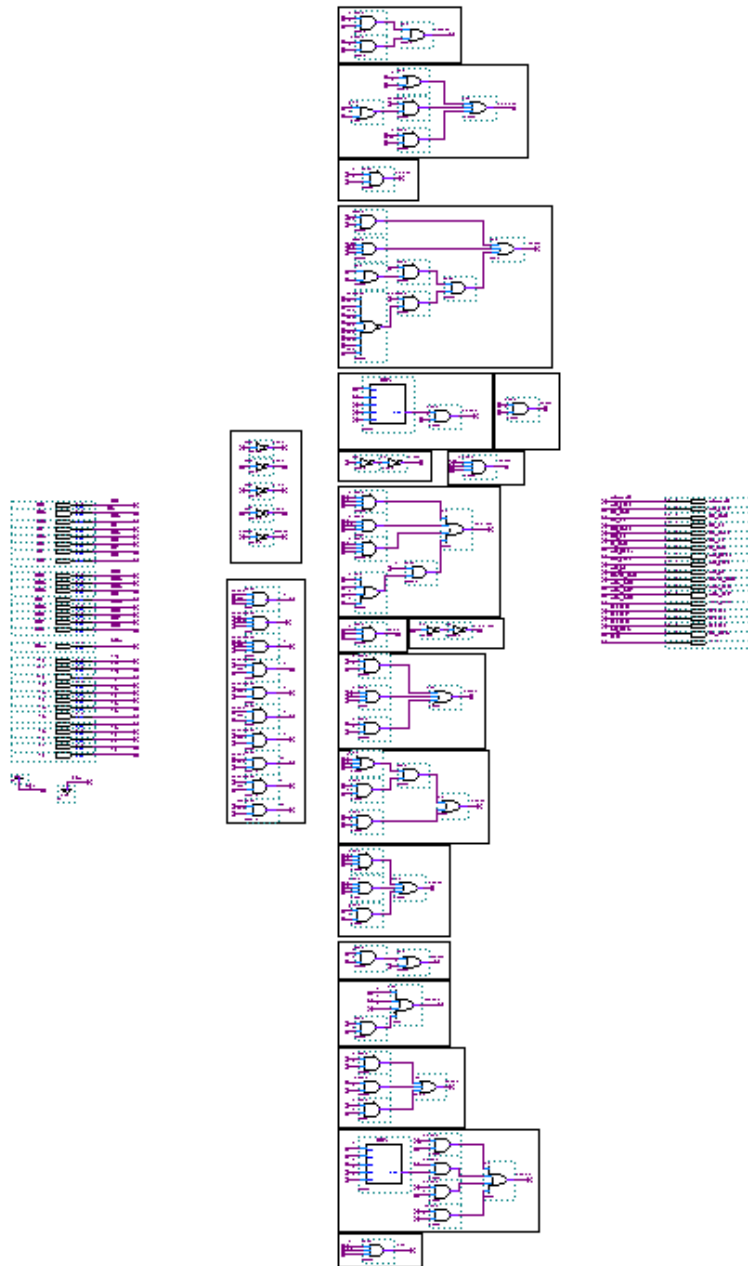


Figure 4: Logic Diagram for the Lab3controller constructed on Quartus

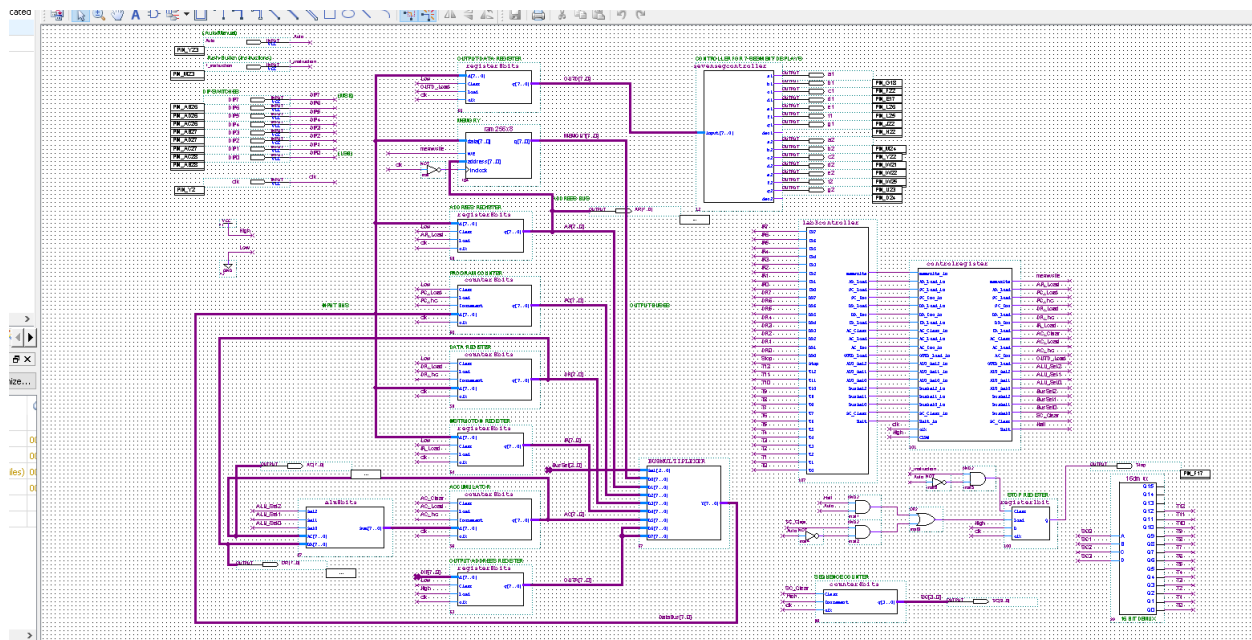


Figure 5: Logic Diagram for the Lab3top constructed on Quartus

- Discussion of used components:** In order to understand how to construct the lab3controller circuit, we had to complete the pre-lab work for hardware. Utilizing the given table of values attached to our lab instructions, we were able to formulate the required equations to create their corresponding circuits (see fig. 4). We then constructed the whole circuit and assigned the pins with their respective input and output values. After compilation and simulation of our waveform diagrams (see fig. 7), we utilized the Altera DE2-115 board to analyze our results and compare them to the expected results.
- Discussion of actual solution:** Upon implementation of the lab3top circuit, we utilized various gates and multiplexers in our designs. We learned how to wirelessly connect input and output values which made construction a lot simpler and more efficient. We utilized box outliners to organize all our designs efficiently. We constructed them in order as listed from top to bottom. We started with all the x and y values and utilized them to construct the actual circuits. Our design proved to be successful after compilation and further simulation analysis.
- Discussion of challenging problems:** During implementation and simulation we did not encounter any serious issues but rather just naming issues. Our compilation was successful, and we were able to successfully assign all the required input and output values their pin assignments. We also did not encounter any problems with our mif file. Our issues appeared in our waveform simulation diagram and prevented us from progressing any further in our laboratory experiment.

Simulation and Verification of Real Implementation

- Simulation and Synthesis results:

Entity: yclone IV E: EP4CE115F29C7
lab3top 229 (0) 80 (0)

Compilation: Task: Compile Design, Analysis & Synthesis, Fitter (Place & Route), Assembler (Generate programming files), TimeQuest Timing Analysis, EDA Netlist Writer, Program Device (Open Programmer)

Status	From	To	Assignment Name	Value	Enabled	Entity	Comment	Tag
10	✓	OUT	AR[0]	Location	PIN_G19	Yes		
11	✓	OUT	AR[1]	Location	PIN_F19	Yes		
12	✓	OUT	AR[2]	Location	PIN_E19	Yes		
13	✓	OUT	AR[3]	Location	PIN_F21	Yes		
14	✓	OUT	AR[4]	Location	PIN_F18	Yes		
15	✓	OUT	AR[5]	Location	PIN_E18	Yes		
16	✓	OUT	AR[6]	Location	PIN_J19	Yes		
17	✓	OUT	AR[7]	Location	PIN_H19	Yes		
18	✓	IN	Auto	Location	PIN_Y23	Yes		
19	✓	OUT	b1	Location	PIN_F22	Yes		
20	✓	OUT	b2	Location	PIN_Y22	Yes		
21	✓	OUT	c1	Location	PIN_E17	Yes		
22	✓	OUT	c2	Location	PIN_W21	Yes		
23	✓	OUT	d1	Location	PIN_L26	Yes		
24	✓	OUT	d2	Location	PIN_W22	Yes		
25	✓	IN	DIP0	Location	PIN_AB28	Yes		
26	✓	IN	DIP1	Location	PIN_AC28	Yes		
27	✓	IN	DIP2	Location	PIN_AC27	Yes		
28	✓	IN	DIP3	Location	PIN_AD27	Yes		
29	✓	IN	DIP4	Location	PIN_AB27	Yes		
30	✓	IN	DIP5	Location	PIN_AC26	Yes		
31	✓	IN	DIP6	Location	PIN_AD26	Yes		
32	✓	IN	DIP7	Location	PIN_AB26	Yes		
33	✓	OUT	DR[0]	Location	PIN_J15	Yes		
34	✓	OUT	DR[1]	Location	PIN_H16	Yes		
35	✓	OUT	DR[2]	Location	PIN_J16	Yes		
36	✓	OUT	DR[3]	Location	PIN_H17	Yes		
37	✓	OUT	DR[4]	Location	PIN_F15	Yes		
38	✓	OUT	DR[5]	Location	PIN_G15	Yes		
39	✓	OUT	DR[6]	Location	PIN_G16	Yes		
40	✓	OUT	DR[7]	Location	PIN_H15	Yes		
41	✓	OUT	e1	Location	PIN_L25	Yes		
42	✓	OUT	e2	Location	PIN_W25	Yes		
43	✓	OUT	f1	Location	PIN_J22	Yes		
44	✓	OUT	f2	Location	PIN_L23	Yes		
45	✓	OUT	g1	Location	PIN_H22	Yes		
46	✓	OUT	g2	Location	PIN_D24	Yes		
47	✓	IN	l_instruction	Location	PIN_M23	Yes		
48	✓	IN	clk	Location	PIN_Y2	Yes		
49	✓	OUT	Stop	Location	PIN_F17	Yes		
50	✓	OUT	a1	Location	PIN_G18	Yes		
51	<<new>>	<<new>>	<<new>>					

This cell shows the status of the assignment in the current row.

Figure 6: Pin Assignment of the circuit constructed on Quartus

 


Figure 7: Waveform simulation of the circuit constructed on Quartus

- **Experimental Verification of Circuit Operation:** After successfully simulating our Quartus design, we successfully completed our pin assignment and mif file creation. Our lab could not progress any further as our waveform diagram was not displaying accurate results and we could not find the root of the issue. We inspected all of the values in our design (circuit diagram and mif file) and we were not able to find any mistakes. We refreshed our program, and we still received the same results. We were not able to continue any further in our experiment.

Discussion and Conclusions

We encountered a couple of very miniscule issues and one major issue that prevented us from progressing any further in our lab experiment. We were able to successfully create our circuit design for the hardware portion. This was verified by the successful compilation and TA verification of our equations which we used to construct the circuits. Our pin assignments and mif file were also correct. Our waveform diagram however, would not show the correct values when compiled and simulated. We followed the instructions in the lab manual with the respective end times and time periods. We grouped the required values and assigned their values, but we were not able to acquire the intended results of this experiment. We inspected all the values of the mif file, and circuit construction but found no errors in our implementation. That was the furthest we were able to advance in this experiment.

In this lab experiment we also learned various new things and techniques on the Quartus platform such as being able to wirelessly connect input and output values. This technique helped us organize our circuits as efficiently as possible. The box outliner helped to achieve that as well. We also learned how to utilize a mif file and construct a proper one. In the prelab we also practiced and mastered the ability to formulate proper equations using Boolean algebra laws.

General Conclusion:

Over the course of the 4 lab sessions, we learned various efficient new techniques when utilizing the Quartus II platform. We were able to successfully complete most of the tasks in this laboratory experiment including construction and compilation of our designs. We did however encounter an unsolvable problem with regards to our waveform simulation that halted any further progression in our experiment for this lab.